




Chapter 7: A Primer On Digital Logic

Basic Computer Architecture

Outline

- *Transistors and Gates

 

- *Combinational Logic

- * Sequential Logic

- * SRAM/ DRAM Cells

Disclaimer: This chapter is only to



get a high level overview ...

- * We assume some **background** in logic gates, transistors, combinational and sequential logic
- * The **aim** of this chapter is to only provide a high level overview
- * For a **deeper** understanding consult any of the classic textbooks on digital logic

Atoms and Molecules of Circuits

The Transistor




- It is just a **switch**.
- It is either switched **on** (current can flow), or switched **off** (no current flow)

How is a Transistor Made?


- * It is made of **Silicon**
 - * Silicon is a semi-conductor (neither conductor or insulator).
 - * We can change its properties:
 - * Add a little bit of impurities → **doping**
- * Dope it with Group III **elements** (3 valence electrons)
 - * Boron, Aluminum and Gallium
 - * It is called a **p-type** semiconductor
- * Or, dope it with Group V **elements** (5 valence electrons)
 - * Phosphorus or Arsenic
 - * It is called a **n-type** semiconductor

Silicon Lattice

 


- * This is a typical silicon lattice. Each Si atom is connected to 4 other atoms via covalent bond

P-Type Doping

 


- * If there is a Boron atom in the **lattice**. It will create bonds with the rest of the atoms.
- * There will be one less electron (**hole**)
- * Holes can **flow**. They are associated with +ve charge. (see the animation)

N-Type Doping

 

- * If there is a Phosphorus atom in the **lattice**. It will create bonds with the rest of the atoms.
- * There will be one more electron (**electron**)
- * Electrons can **flow**. They are associated with -ve charge. (see the animation)


Let us make a transistor.

 

- * NMOS transistor → Put two **n-type** wells in a **p-type** substrate
- * Now, assume that we apply **+ve** charge to the gate.
- * Channel → This forms because electrons move towards the positive charge. Forms a conductive layer that can conduct **current**.


NMOS Transistor

Metal-Oxide-Semiconductor

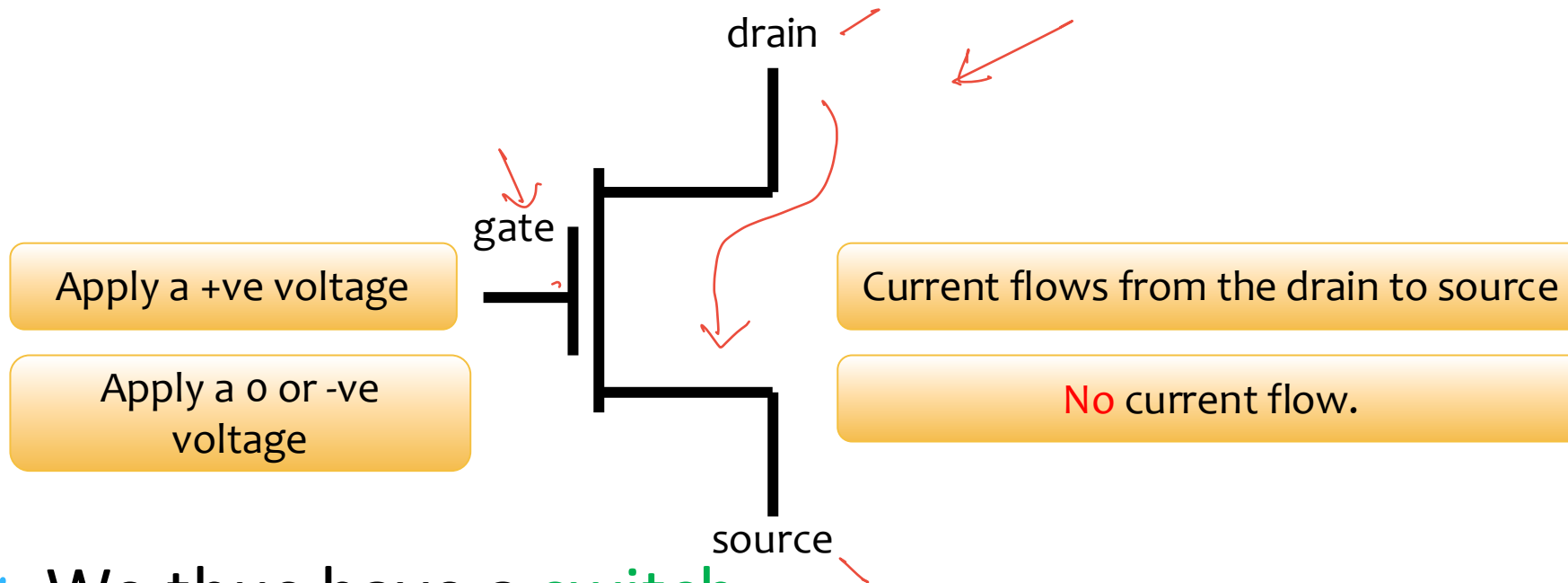


- * We thus have a **switch**
 - * Apply a **+ve** voltage at the gate → make the transistor conduct
 - * Apply a **-ve** or 0 voltage at the gate → transistor is off (no current flow across it)

PMOS Transistor

 

- * PMOS transistor → Put two **p-type** wells in an **n-type** substrate
- * Now, assume we apply **0 or -ve** charge to the gate.
- * Channel → This forms because holes move towards the gate. This channel can conduct **current**.


PMOS Transistor

 

* We thus have a **switch**

- * Apply a **+ve** voltage at the gate → transistor is off (no current flow across it)
- * Apply a **-ve** or 0 voltage at the gate → transistor conducts

Let us make an inverter


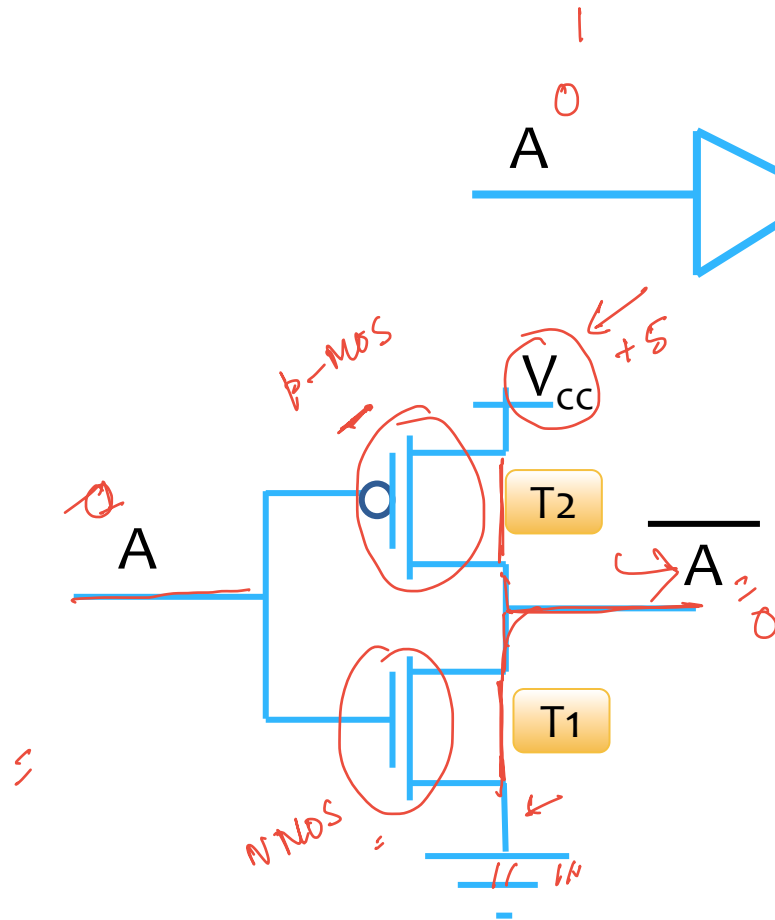


If $A = 1$ (+ve voltage)
T1 is on, T2 is off
Thus, the output will be connected to the ground, and it will be a logical 0

If $A = 0$ (0 voltage)
T1 is off, T2 is on
Thus, the output will be connected to the supply (V_{CC}), and it will be a logical 1

Complementary Metal-Oxide-Semiconductor


NOR Gate

  

A	B	T1	T2	T3	T4	Out
0	0	off	off	on	on	1
1	0	on	off	off	on	0
0	1	off	on	on	off	0
1	1	on	on	off	off	0






NAND		O/P
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate

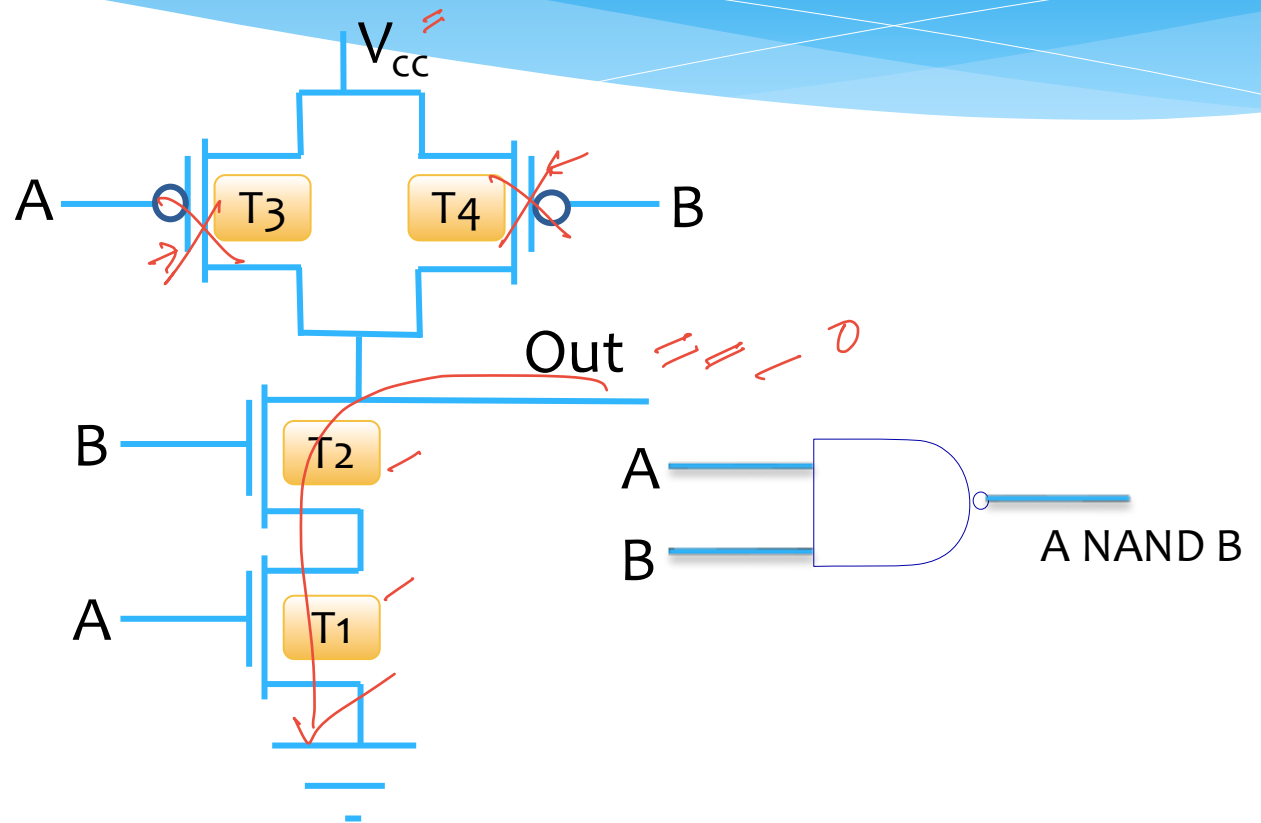


A	B	T1	T2	T3	T4	Out
0	0	off	off	on	on	1
1	0	on	off	off	on	1
0	1	off	on	on	off	1
1	1	on	on	off	off	0

Summary of Logic Gates

     

Outline


 
- *Transistors and Gates
- *Combinational Logic
- * Sequential Logic
- * SRAM/ DRAM Cells




Multiplexer

Given n **inputs**, choose one based on the **select** bits.

 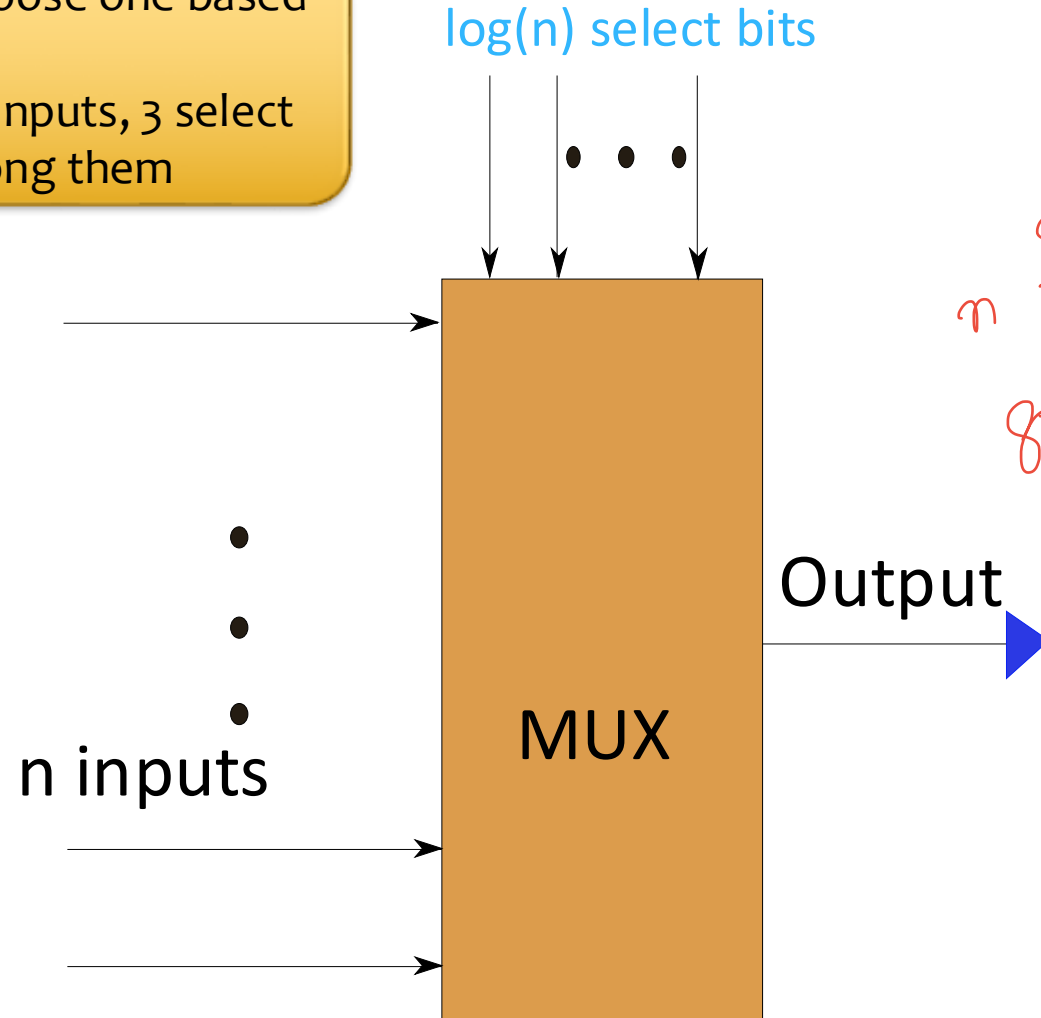Example: Given 8 inputs, 3 select bits, choose 1 among them



Design of a Multiplexer

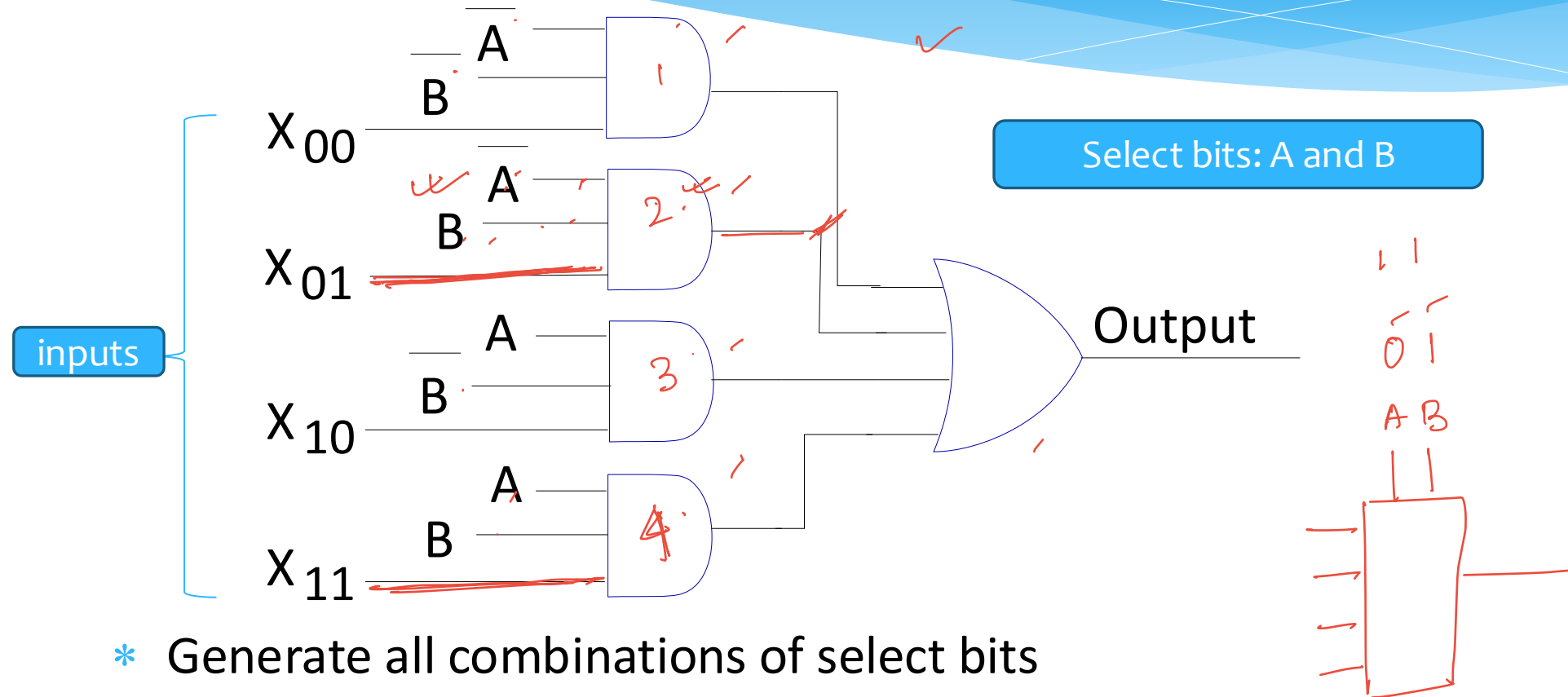

* Generate all combinations of select bits

* $\bar{A} \cdot \bar{B}, A \cdot \bar{B}, \bar{A} \cdot B, A \cdot B$


* Only one of the combinations is true.

* For this combination the output of the AND gate is equal to the input (X_{AB}), rest of the outputs of the AND gates are 0


* The output is equal to $(X_{AB} \text{ OR } 0 \text{ OR } 0 \text{ OR } 0) = X_{AB}$

Demultiplexer

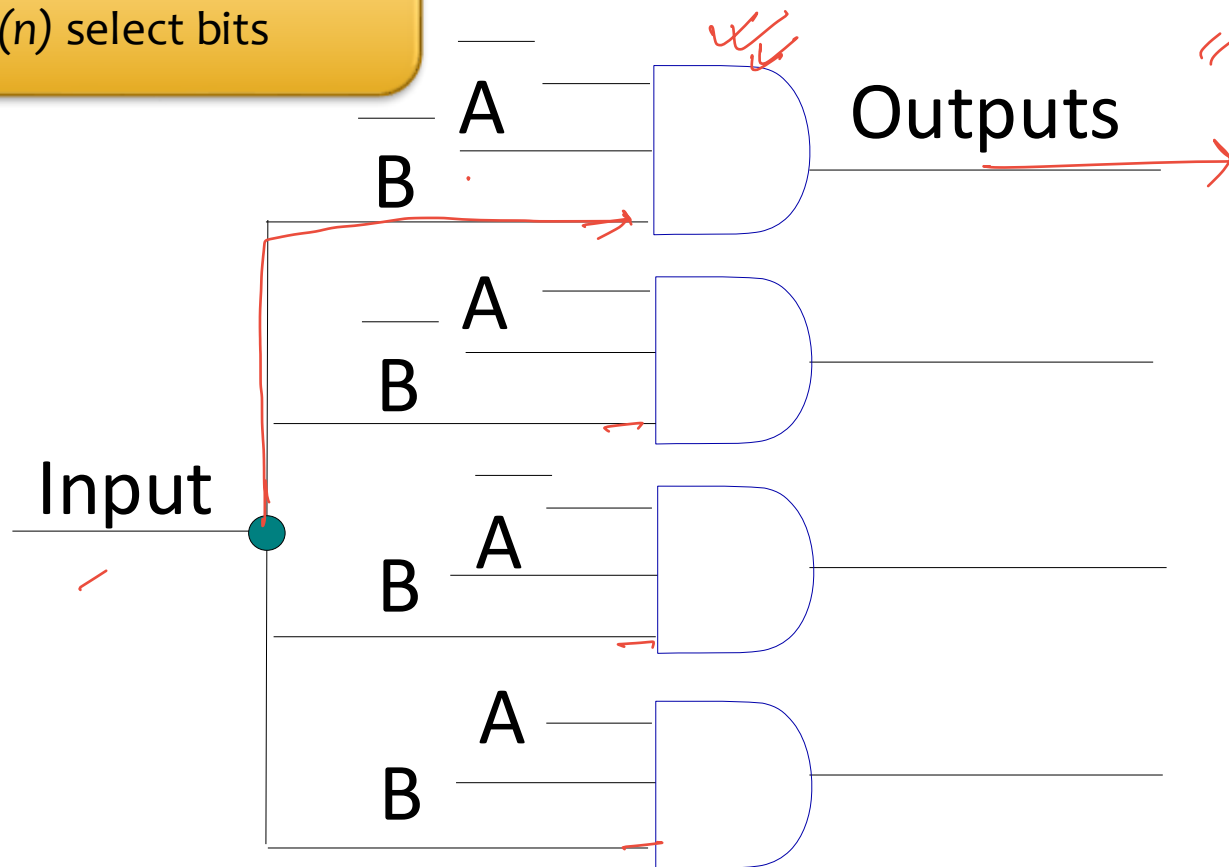Given 1 **input**, make it appear on one of n outputs. The output is decided by $\log(n)$ select bits



A B
0 0

 


Working of a Demultiplexer

- * Same logic
 - * Generate all combinations of A, B, \bar{A} , and \bar{B}
 - * Only one combination is TRUE
 - * The output of that AND gate is equal to: $X \text{ AND } 1 = X$
Here, X is the input
 - * The outputs of the rest of the AND gates are 0

Decoder

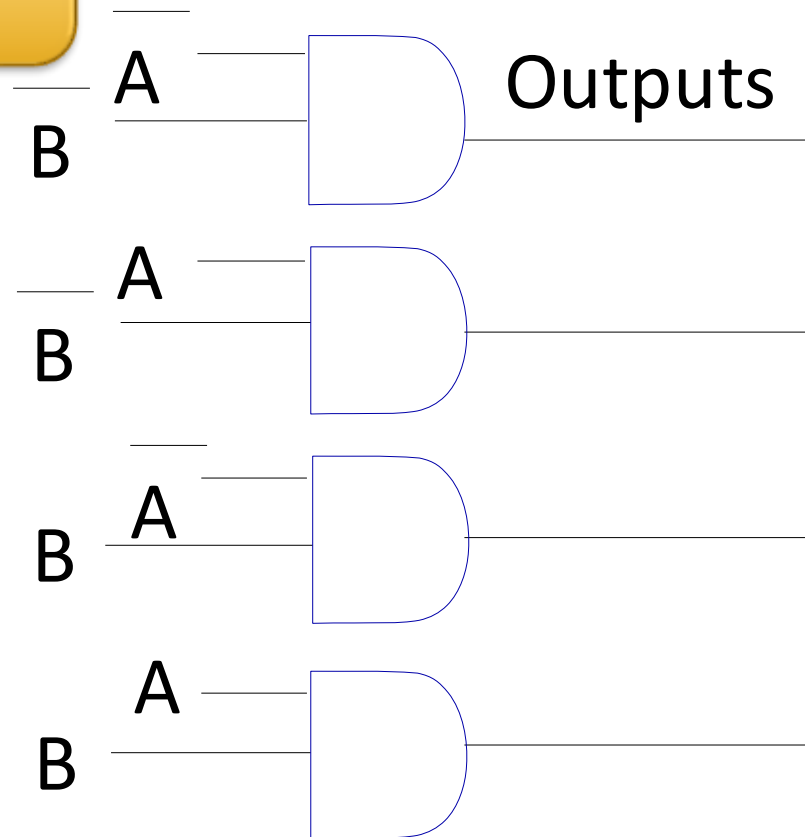
Set one of the n outputs to 1. The output is decided by $\log(n)$ select bits



Operation is similar to a demultiplexer

Encoder

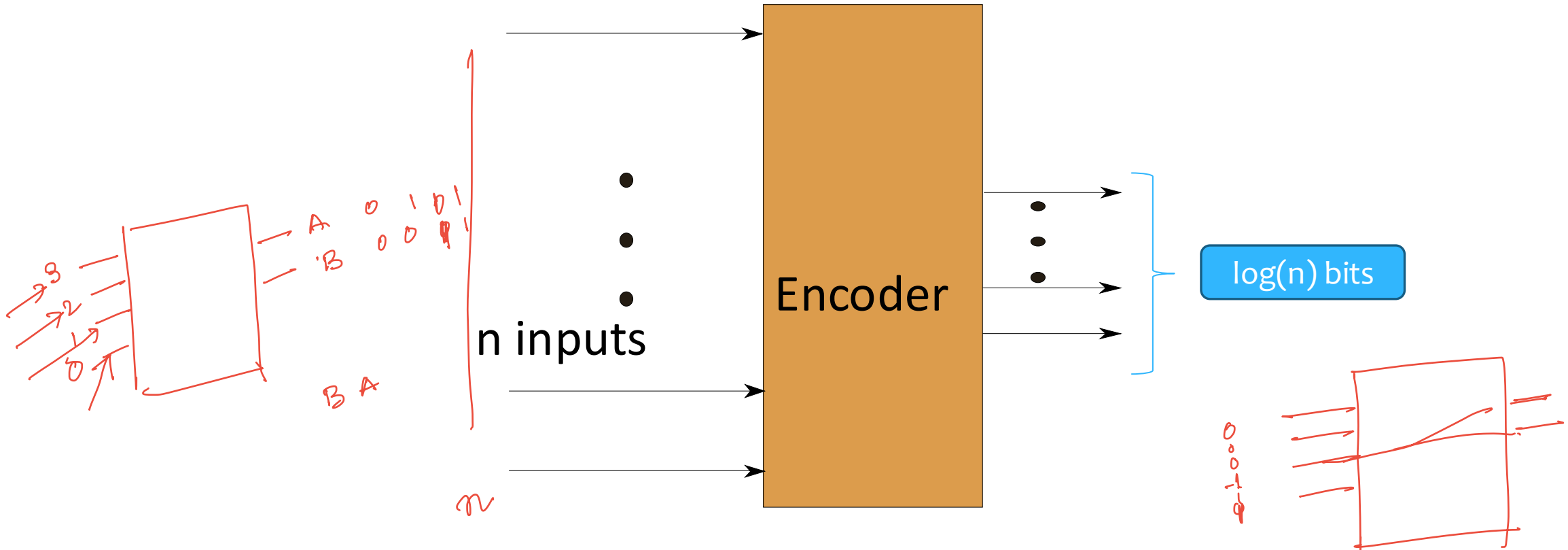Given n inputs, assume only one of them is 1. Find its id.
For example: if the 6th input out of 8 inputs is 1. The output should be 110



Example of a 3-bit Encoder

Output bits

Input bit	Bit2	Bit1	Bit0
b0	0	0	0
b1	0	0	1
b2	0	1	0
b3	0	1	1
b4	1	0	0
b5	1	0	1
b6	1	1	0
b7	1	1	1


Here, the + symbol
stands for OR

$$\text{Bit2} = b4 + b5 + b6 + b7$$

$$\text{Bit1} = b2 + b3 + b6 + b7$$


$$\text{Bit0} = b1 + b3 + b5 + b7$$

Example of a 3-bit Encoder - II

 

Outline

 - * Transistors and Gates
- * Combinational Logic
- * Sequential Logic
- * SRAM/ DRAM Cells




S-R latch
 S: Set
 R: Reset

$S=1 \quad R=0$
 $S=0 \quad R=1$
 $S=0 \quad R=0$
 $S=1 \quad R=1$

$Q=1 \quad \bar{Q}=0$ - Set
 $Q=0 \quad \bar{Q}=1$ - Reset
 maintain Old values.
 X not desired state
 
$$\overline{1 \cdot \bar{Q}} = \bar{1} + \bar{\bar{Q}} = 0 + Q = Q$$



$$\overline{1 \cdot Q} = \bar{1} + \bar{Q} = 0 + \bar{Q} = \bar{Q}$$

cross-coupled pair (latch)

NAND


0	0	1
0	1	1
1	0	1
1	1	0

At least one i/p = 0
 \hookrightarrow o/p = 1

SR Latch



 Use a cross-coupled pair of NAND gates to store a stable value.



$S \rightarrow \text{Set}$

$R \rightarrow \text{Reset}$

* $S = 1, R = 0, Q = 1$

* $S = 0, R = 1, Q = 0$


* $S = 0, R = 0, \text{<maintain old values>}$

Set the
values



Understand
these points

Clocked SR Latch

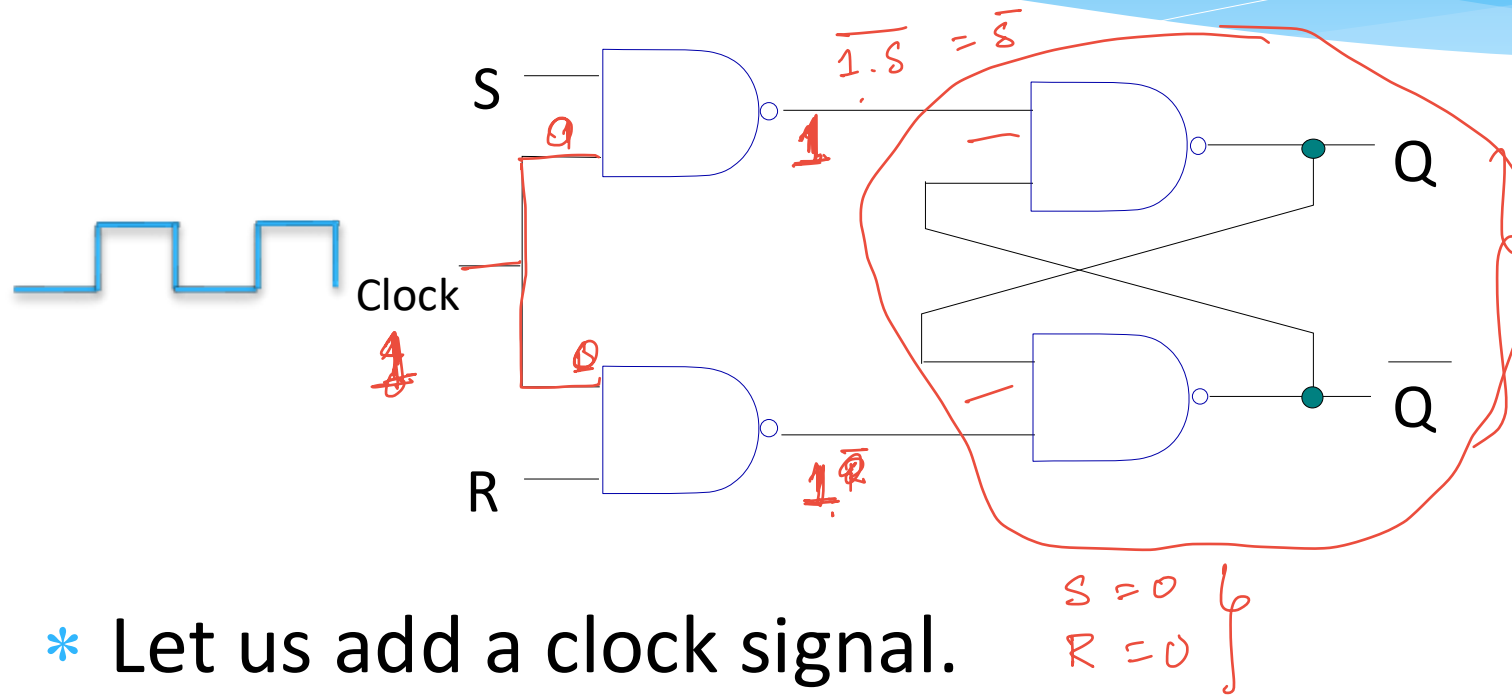

$$freq = \frac{1}{\text{clock period}}$$

$$200 \text{ kHz}$$

$$S=1 \quad R=0$$

* Let us add a clock signal.

- * When the clock is 1, outputs of the NAND gates are \bar{S} and \bar{R} respectively (same as the classic SR latch)
- * Clock is 0 \rightarrow they are 1 and 1 respectively (maintain old values)

